

B. Tech 2nd Semester Examination
Principles of Electrical Engineering (CBS)

EE-101

Time : 3 Hours

Max. Marks : 60

The candidates shall limit their answers precisely within the answer-book (40 pages) issued to them and no supplementary/continuation sheet will be issued.

Note : Attempt five question selecting one question from each of the section A, B, C and D. Question 9 in section E is compulsory.

SECTION - A

1. (a) Explain power transmission and distribution via overhead lines. (6)
- (b) Explain about Steam, Hydel and Nuclear power generation. (6)
2. (a) State Thevenin's theorem and explain the steps involved in the theorem in detail. (6)
- (b) Explain in detail about the loop and nodal methods of analysis. (6)

SECTION - B

3. (a) Draw circuit and vector diagrams, find the expression for impedance, current, phase, angle and power consumed in the R.L Series Circuit. (6)
- (b) Explain clearly how a vector can be represented by a complex number. (6)

4. (a) Explain in detail measurement of power by 2-wattmeter method. (6)
- (b) Derive the value of phase voltages and line voltages in a balanced star connected three phase circuits. (6)

SECTION - C

5. (a) Explain the types of moving iron type instruments in detail. (6)
- (b) Explain the construction and working principle of PMMC instrument (6)
6. (a) What do you understand by
 - (i) Permeability of free space.
 - (ii) Relative permeability.
 - (iii) Absolute permeability. (6)
- (b) Derive a Relationship between field intensity and flux density. (6)

SECTION - D

7. (a) Draw the Phasor diagram on no load and full load of the transformer. (6)
- (b) Explain the working principle and construction of single phase auto-transformers. (6)
8. (a) Explain the working principle of single phase induction motor. (6)
- (b) Explain the speed control of D.C. motors and D.C motor starters. (6)

SECTION - E

9. (a) Define Kirchhoff's laws.
(b) State superposition theorem.
(c) Explain maximum power transfer theorem.
(d) Define power factor.
(e) Define m.m.f.
(f) Define reluctance.
(g) Define the term voltage regulation for a single phase transformer.
(h) Define active power, apparent power.
(i) Define Q factor for the series resonant circuit.
(j) Define ohm's law.
(k) Define RMS value & average value.
(l) Define reciprocity theorem. (1×12=12)

<https://www.hptuonline.com>

Whatsapp @ 9300930012

Send your old paper & get 10/-

अपने पुराने पेपर्स भेजे और 10 रुपये पायें,

Paytm or Google Pay से